



## Fundamentals of Physics in Engineering I

### Unit 7.- ELECTRIC CURRENT


1.- A copper wire, with a circular cross section of 1 cm of diameter, carries a current of 100 A. Copper has  $8.5 \times 10^{22}$  free electrons per  $\text{cm}^3$  and its resistivity at ambient temperature is  $1.72 \times 10^{-8} \Omega\text{m}$ . Calculate: (a) The current density in the wire in  $\text{A/m}^2$ . (b) The drift velocity of the free electrons. (c) The value of the electric field inside the wire.

2.- Find the density of free electrons  $n$  for a copper wire if there is a free electron for each copper atom. If the maximum recommended current for a copper wire of 0.81 mm of radius (as the ones used domestically) is 15 A, what is the drift velocity of the electrons in the wire?


3.-A copper wire has a circular section of 1.02 mm of diameter and carries a current of 1.67 A. The resistivity is  $1.72 \times 10^{-8} \Omega\text{m}$  at a temperature of  $20^\circ\text{C}$ . Calculate, at  $20^\circ\text{C}$ : (a) The electric field inside the wire. (b) The potential difference between two points separated 50 m along the wire. (c) The resistance of a copper wire with a length of 50 m. (d) The resistance at  $0^\circ\text{C}$  and  $100^\circ\text{C}$ , if the temperature coefficient of resistivity of copper is  $\alpha = 0.00393 (^\circ\text{C})^{-1}$ .

4.-Two identical resistors are connected in series to a potential difference of  $V$ . Later on, the two resistors are connected in parallel to the same potential difference  $V$ . Which one of the two set-ups dissipates more power?

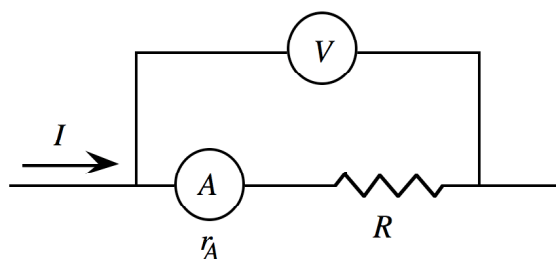5.-An ammeter with resistance  $r_A$  is connected in series with a resistor, whose resistance  $R$  we want to measure, and a voltmeter is connected in parallel with the set, as can be seen in the figure. (a) Calculate  $R$  as a function of the values  $I_m$  and  $V_m$  measured by the ammeter and the voltmeter, respectively. (b) Calculate  $R$  when  $V_m/I_m \gg r_A$ . (c) If  $V_m = 23 \text{ V}$ ,  $I_m = 62 \text{ mA}$  and  $r_A = 14 \Omega$ , which is the value of  $R$ ?



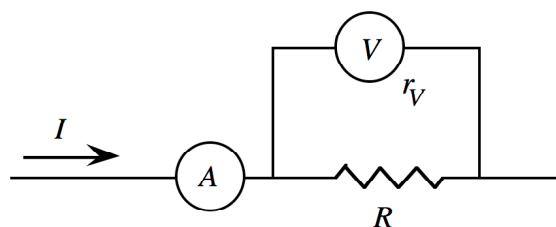6.-A voltmeter with resistance  $r_V$  is connected in parallel with a resistor, whose resistance  $R$  we want to measure, and an ammeter is connected in series with the set, as can be seen in the figure. (a) Calculate  $R$  as a function of the values  $I_m$  and  $V_m$  measured by the ammeter and the voltmeter, respectively. (b) Calculate  $R$  when  $V_m/I_m \ll r_V$ . (c) If  $V_m = 43 \text{ V}$ ,  $I_m = 16 \text{ mA}$  and  $r_V = 62 \text{ M}\Omega$ , which is the value of  $R$ ?



7.-Dynamic resistance,  $R_{din} = dV/dI$ , is a useful concept when non-ohmic circuit components are studied. For a diode, a simple model for the  $pn$  junction behaviour predicts a current-voltage relationship in the form  $I(V) = I_0[\exp(eV/kT) - 1]$ , where  $I_0$  is the saturation current, different for each diode,  $k$  is the Boltzmann's constant,  $T$  is the absolute temperature and  $e$  is the electron charge. Obtain an expression for the dynamic resistance of this device.

## **BIBLIOGRAPHY**

H. D. Young, R. A. Freeman, “Física universitaria (Sears-Zemansky)” (vol. 2), Pearson Educación, México (2009).

W. E. Gettys, F. J. Keller, M. J. Skove, “Física clásica y moderna”, McGraw-Hill, Madrid (1991).

F. A. González, “La física en problemas”, Editorial Tébar-Flores, Madrid (1995).

P. A. Tipler, G. Mosca, “Física para la ciencia y la tecnología” (vol. 2), Reverté, Barcelona (2009).

C. Carnero, J. Aguiar, J. Carretero, “Problemas de física II. Electromagnetismo”, Editorial Ágora, Málaga (1996).

J. Llinares, A. Page, “Curso de física aplicada: electromagnetismo y semiconductores”, Servicio de Publicaciones, Universidad Politécnica de Valencia, Valencia (1987).