


COMPUTERS ORGANIZATION

2ND YEAR COMPUTE SCIENCE MANAGEMENT ENGINEERING

UNIT 3 - ARITHMETIC-LOGIC UNIT

JOSÉ GARCÍA RODRÍGUEZ


JOSÉ ANTONIO SERRA PÉREZ

 

ALU


Arithmetic Logic Unit

 - ◆ Introduction
- ◆ Logic Operations
- ◆ Addition and subtraction
 - ◆ Carry propagated adder (CPA)
 - ◆ Adder-Subtractor circuit
 - ◆ Overflow
 - ◆ Carry Look-ahead Adder (CLA)
- ◆ Multiplication
 - ◆ Binary multiplication without sign
 - ◆ Binary multiplication with sign
 - ◆ Booth Algorithm
- ◆ Division
- ◆ Conclusions




Introduction

Introduction

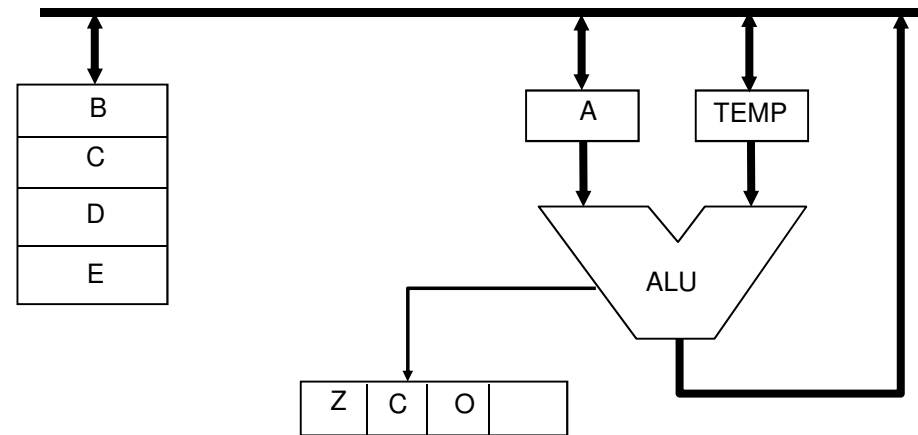

 
- ◆ Arithmetic and logic operator (one or more)
- ◆ Accumulator
- ◆ One or more temporal registers
- ◆ Result flags
 - ◆ Carry (C)
 - ◆ Negative (N)
 - ◆ Overflow (O or V)
 - ◆ Zero (Z)




Logic Operations

Logic operations

 - ◆ Easy to implement \Rightarrow Direct correspondence with the Hardware.
- ◆ Logic gates AND, OR, XOR, INVERTER,...



 

Half-adder



Addition and subtraction

Binary half-adder (H.A.)

Inputs		Outputs	
X	Y	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1


$$S = \overline{X} \cdot Y + X \cdot \overline{Y} = X \oplus Y$$

$$C = X \cdot Y$$

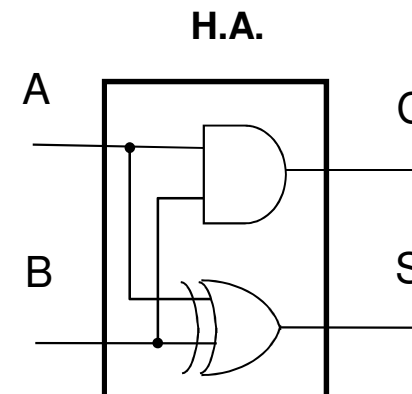 



Addition
and
Subtraction

 

Full Adder (F.A.)


Inputs			Outputs	
A	B	Cin	S	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$S = \bar{A} \cdot \bar{B} \cdot Cin + \bar{A} \cdot B \cdot \bar{Cin} + A \cdot \bar{B} \cdot \bar{Cin} + A \cdot B \cdot Cin$$

$$Cout = A \cdot B + A \cdot Cin + B \cdot Cin$$

$$S = (A \oplus B) \oplus Cin$$


$$Cout = AB + Cin(A \oplus B)$$

 


Addition
and
Subtraction

Full Adder (F.A.)

- Usign half-adders (H.A.)

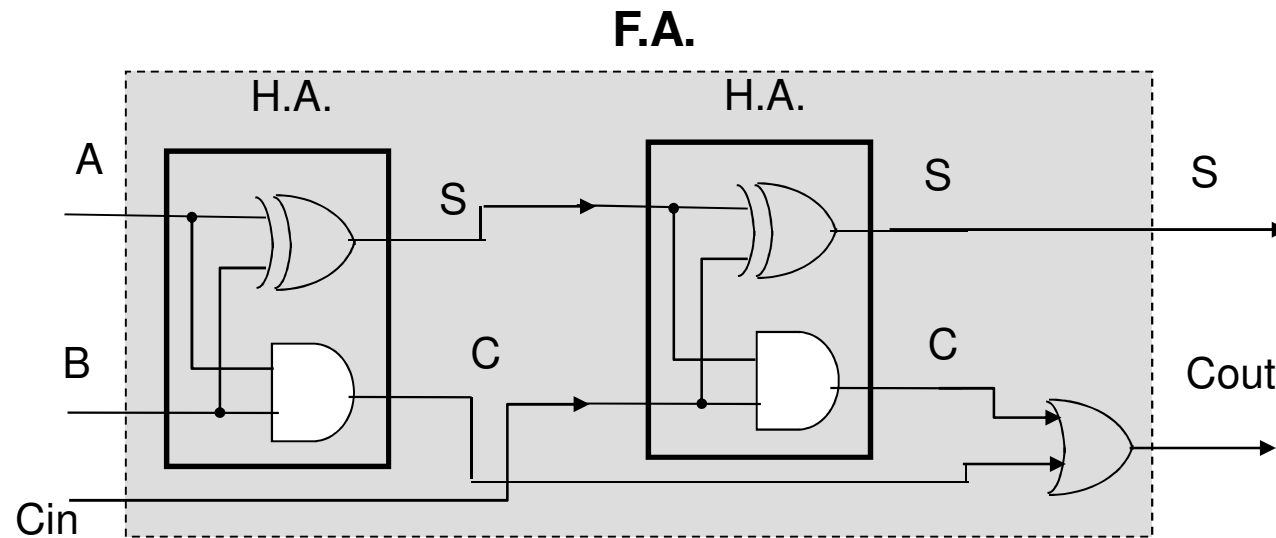


 

Addition
and
Subtraction

- Usign gates

Full Adder (F.A.)

 




Addition
and
Subtraction

Carry Propagated Adder

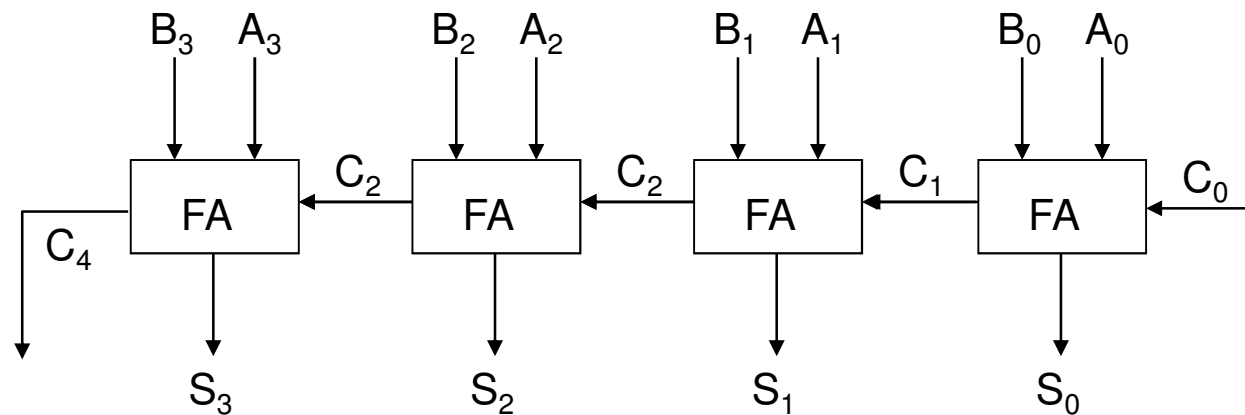- ◆ To add two numbers of n bits, n full adder should be placed one after another.
- ◆ Carry is propagated from one stage to the next one: Carry Propagated Adder.






Addition
and
Subtraction


Carry Propagated Adder

- ◆ Adders built with logic gates using the expression:

$$S = \bar{A} \cdot \bar{B} \cdot Cin + \bar{A} \cdot B \cdot \overline{Cin} + A \cdot \bar{B} \cdot \overline{Cin} + A \cdot B \cdot Cin$$
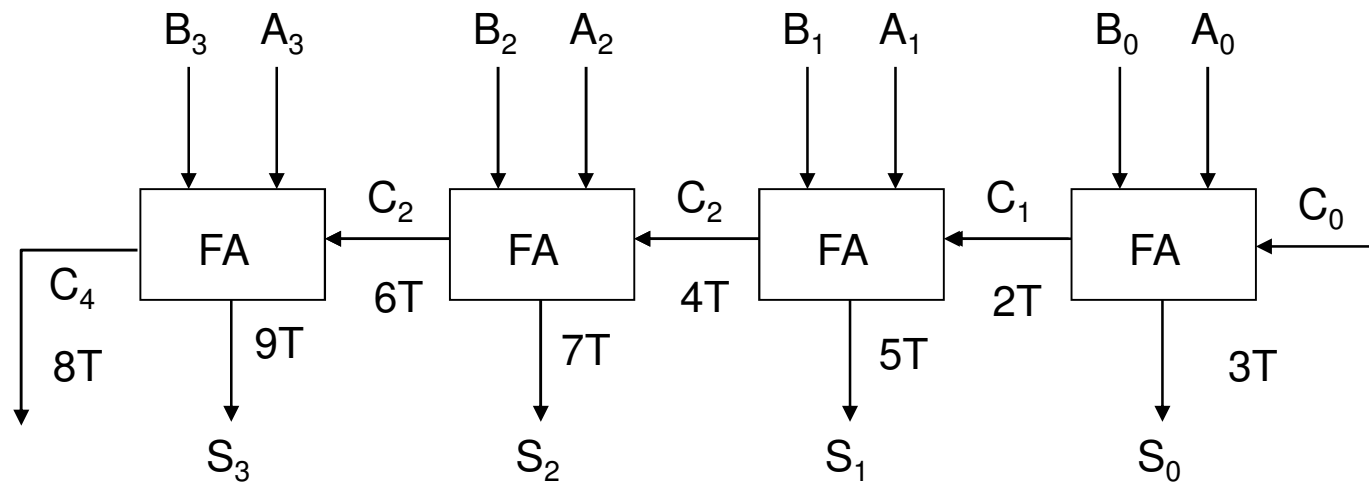
$$Cout = A \cdot B + A \cdot Cin + B \cdot Cin$$





 


Addition
and
Subtraction

Carry Propagated Adder

- ◆ Full adders built with half-adders

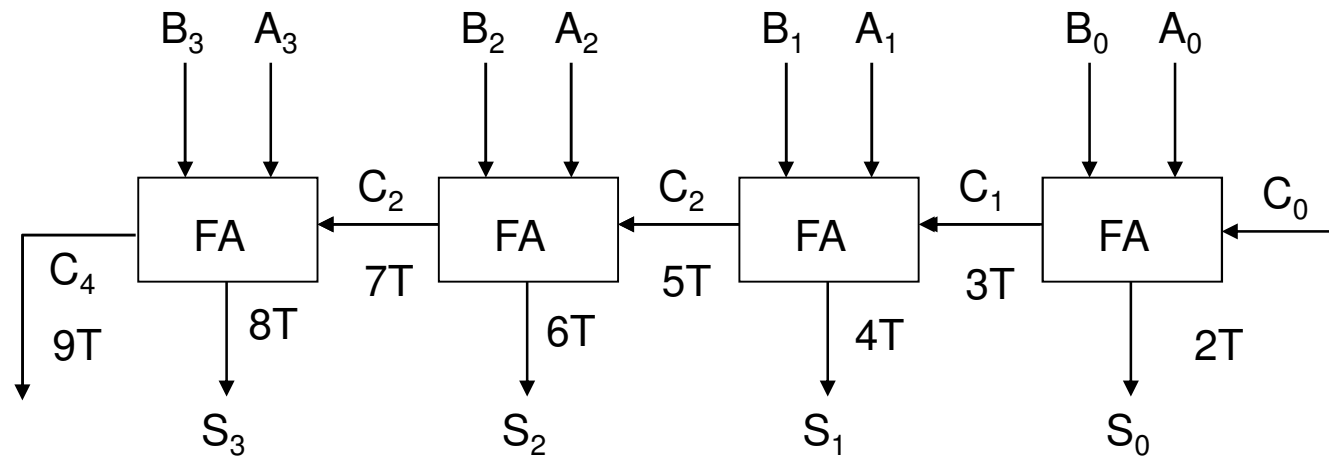 


$$Total_Time = (2 \cdot n + 1)T$$

 


Addition
and
Subtraction

Subtractor circuit

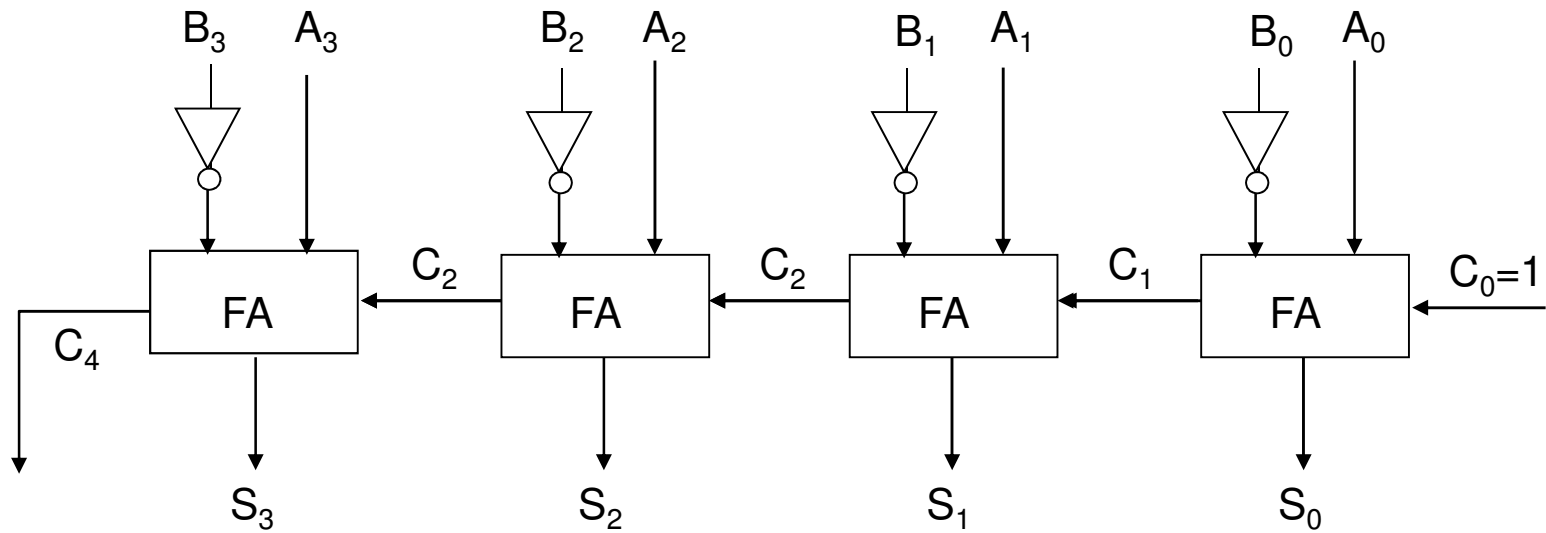- ◆ The circuit works with numbers in two's complement notation.
- ◆ $A - B = A + (C1(B) + 1)$



 



Addition
and
Subtraction

Adder-Subtractor Circuit

S/A	B _i	FA input
0	0	0
0	1	1
1	0	1
1	1	0

$$Total_Time = 2(n+1)T$$

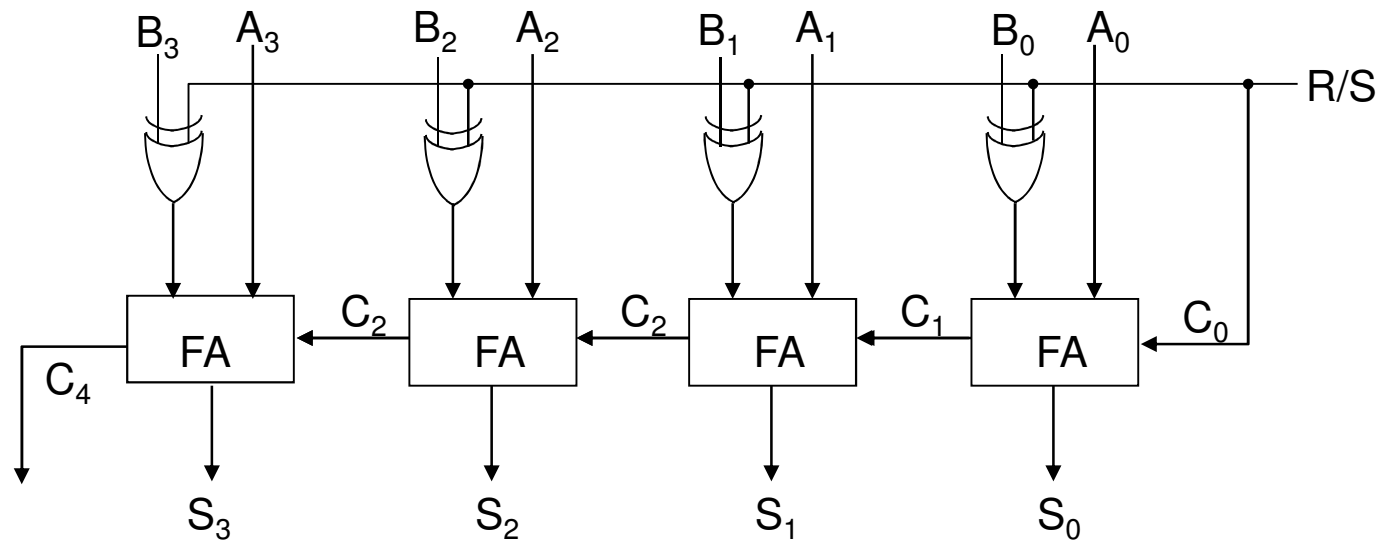


 


Addition
and
Subtraction

Overflow detection

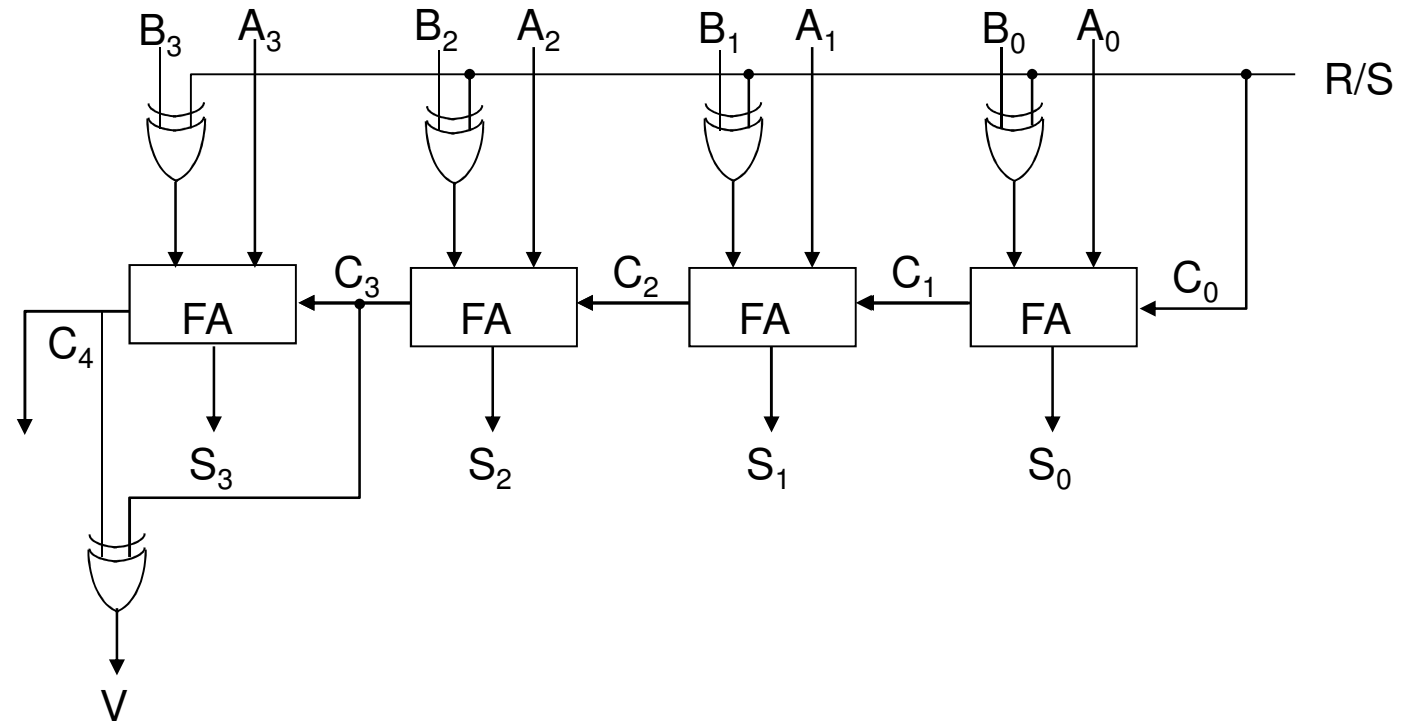Two's complement Adder-Subtractor with
overflow detection



 

Addition
and
Subtraction

Carry Look-ahead Addder

- ◆ Assume A and B to be 4 bits numbers
- ◆ Carry generating signal: $G_i = a_i \cdot b_i$
- ◆ Carry propagating signal: $\begin{cases} P_i = a_i \oplus b_i \\ P_i = a_i + b_i \end{cases}$
- ◆ Carry on stage i: $C_i = G_i + P_i \cdot C_{i-1}$
- ◆ Characterized for A and B:

$$C_0 = G_0 + P_0 \cdot C_{-1}$$

$$C_1 = G_1 + P_1 \cdot C_0$$

$$C_2 = G_2 + P_2 \cdot C_1$$

$$C_3 = G_3 + P_3 \cdot C_2$$



Addition
and
Subtraction

Carry Look-ahead Addder

- ◆ Expanding the expressions depending on C_{-1} :


$$C_0 = G_0 + P_0 \cdot C_{-1}$$

$$C_1 = G_1 + P_1 \cdot G_0 + P_1 \cdot P_0 \cdot C_{-1}$$

$$C_2 = G_2 + P_2 \cdot G_1 + P_2 \cdot P_1 \cdot G_0 + P_2 \cdot P_1 \cdot P_0 \cdot C_{-1}$$


$$C_3 = G_3 + P_3 \cdot G_2 + P_3 \cdot P_2 \cdot G_1 + P_3 \cdot P_2 \cdot P_1 \cdot G_0 + P_3 \cdot P_2 \cdot P_1 \cdot P_0 \cdot C_{-1}$$

 
- ◆ Carries depend on a_i and b_i .
- ◆ These expressions are resolved as addition of products.
- ◆ Three levels of logic gates are needed to get each carry.



Addition
and
Subtraction



Carry Look-ahead Adder

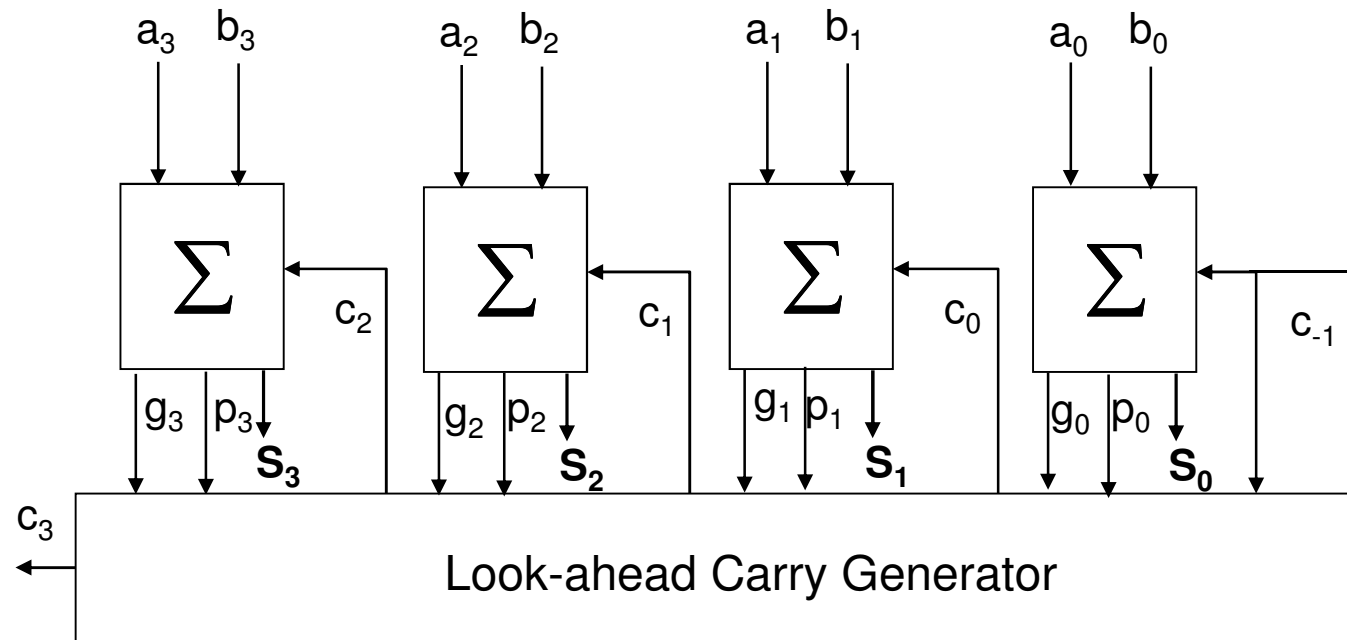

 


Addition
and
Subtraction

Carry Look-ahead Adder

 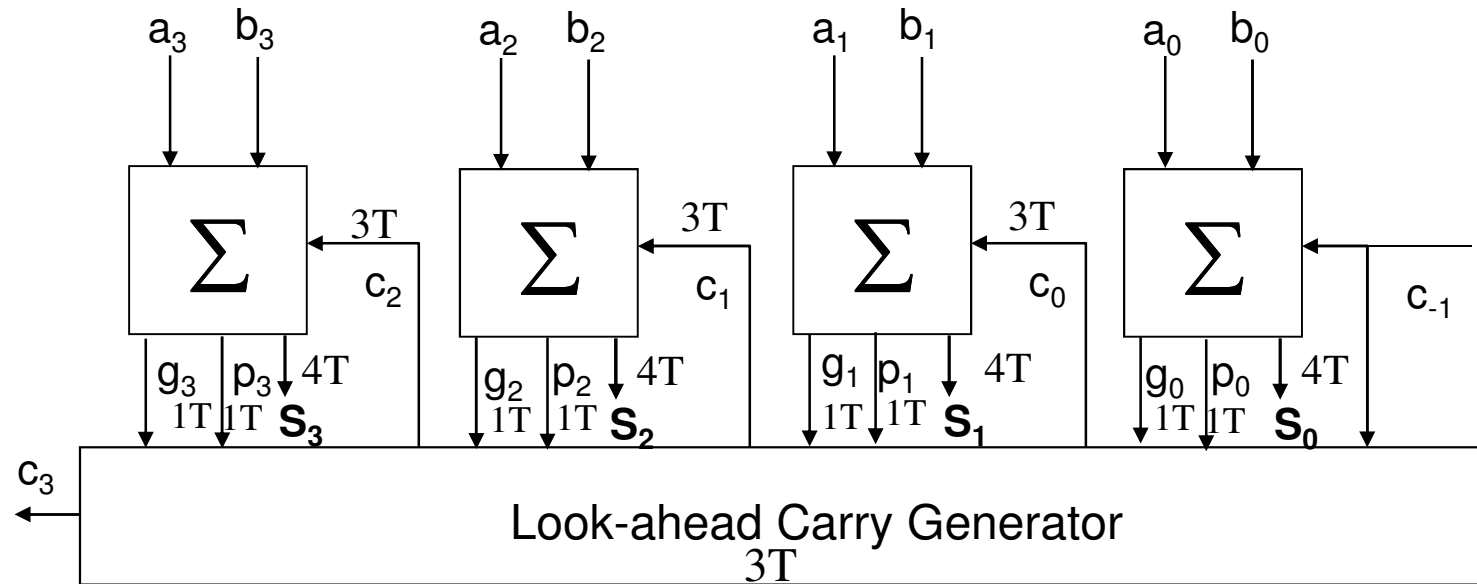


Adders built
with half-adders

 


Addition
and
Subtraction

Example (8 bits CLA)

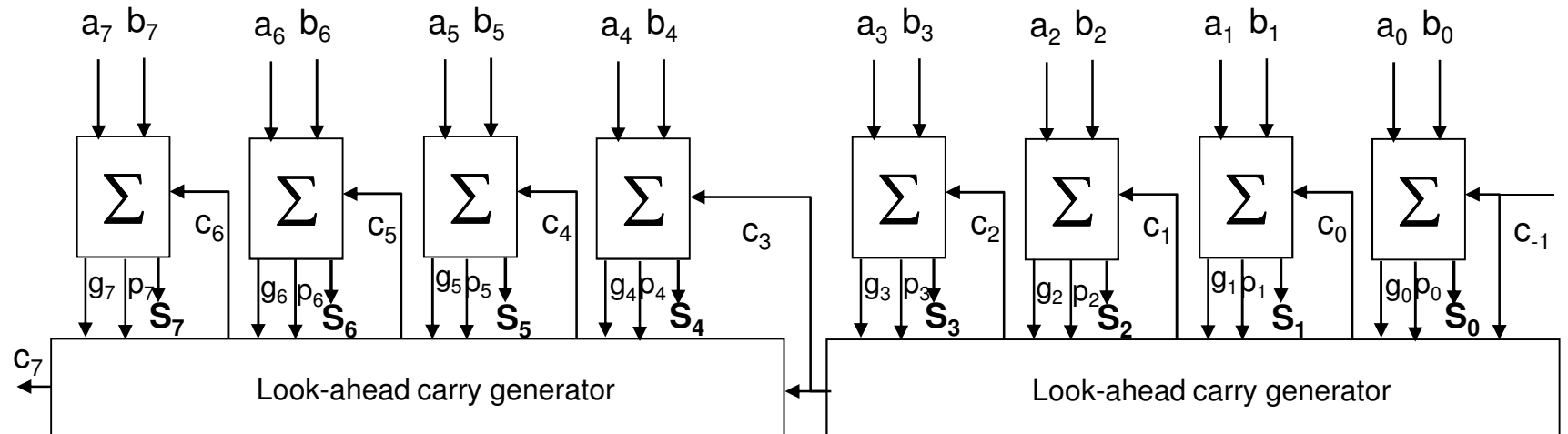


Calculate the delay in this CLA supposing that the adders are built with half-adders.


Compare the result against a 8 bits CPA.

 

Addition and Subtraction

Example (4 bits CLA)

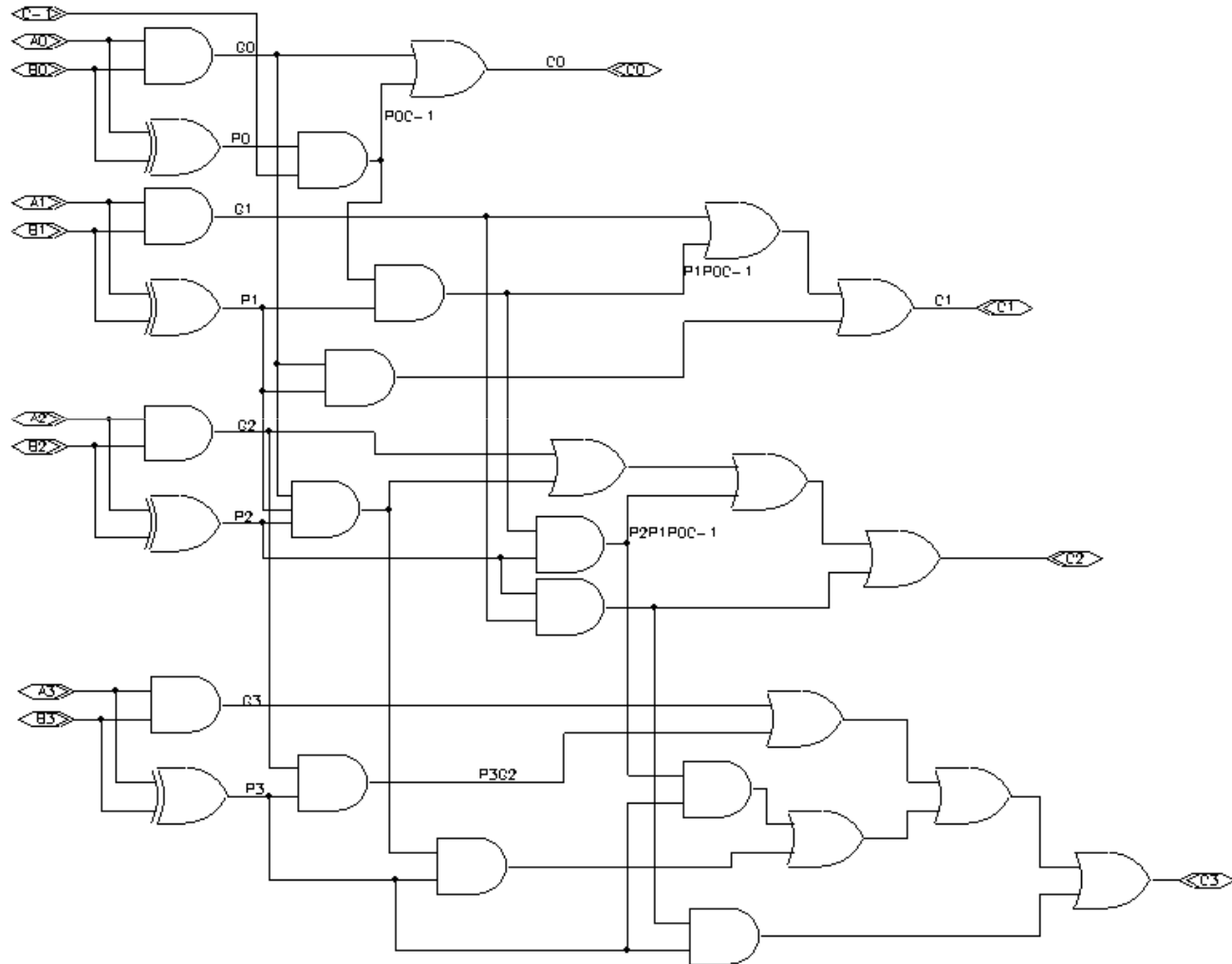


 

Addition
and
Subtraction

Example (4 bits CLA)

C3	C2	C1	C0		C3	C2	C1	C0	
0	1	1	1		1	1	1		
	0	1	1	1		1	0	1	0
	0	1	1	1		1	1	1	1
	1	1	1	0		1	0	0	1

 




Multiplication

Multiplication

- ◆ Sums and shifts algorithm
- ◆ If multiplicand has n bits and multiplier has m bits, then the product will have $n+m$ bits.
- ◆ Binary multiplication: simple as you only multiply by 1 or by 0.

Multiplicand				5	3	2
Multiplier				4	3	1
				<hr/>		
				5	3	2
		1	5	9	6	
	2	1	2	8		
	<hr/>					
Product	2	2	9	2	9	2

 

Multiplication

Binary multiplication without sign

Repeat n times

If bit 0 of multiplier=1 then

Sum the multiplicand to the left half of the product and place the result into the left half of the product


End if

Shift the product register 1 bit to the right

Shift the multiplier register 1 bit to the right

End repeat

*Preliminary
Version*

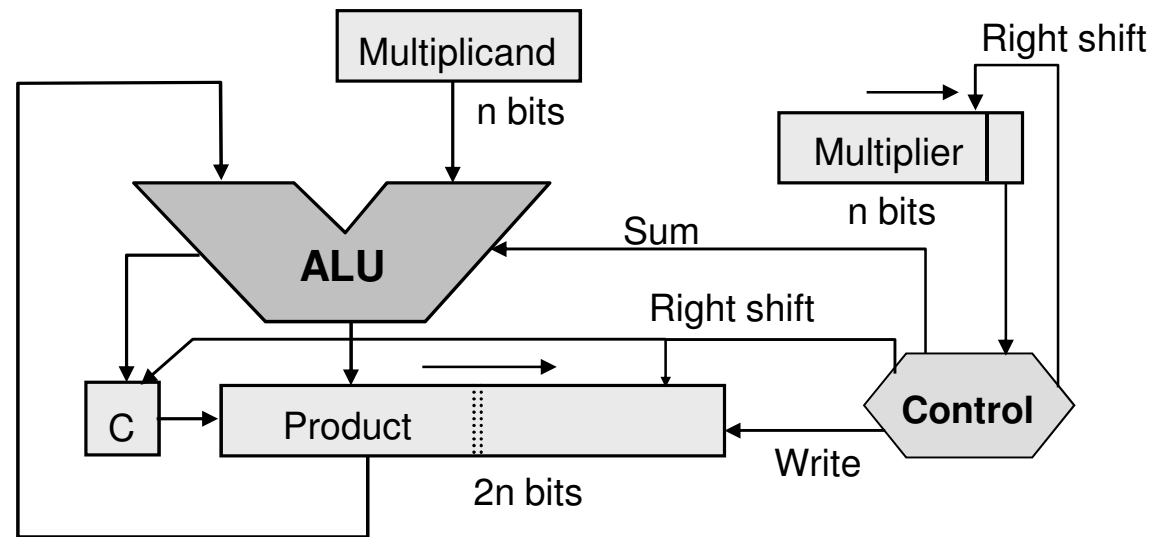




Multiplication

Binary multiplication without sign

Multiplicand	1	0	1	1				
Multiplier	1	1	0	1				
					1	0	1	1
					0	0	0	0
					1	0	1	1
					1	0	1	1
Product	1	0	0	0	1	1	1	1

*Preliminary
Version*

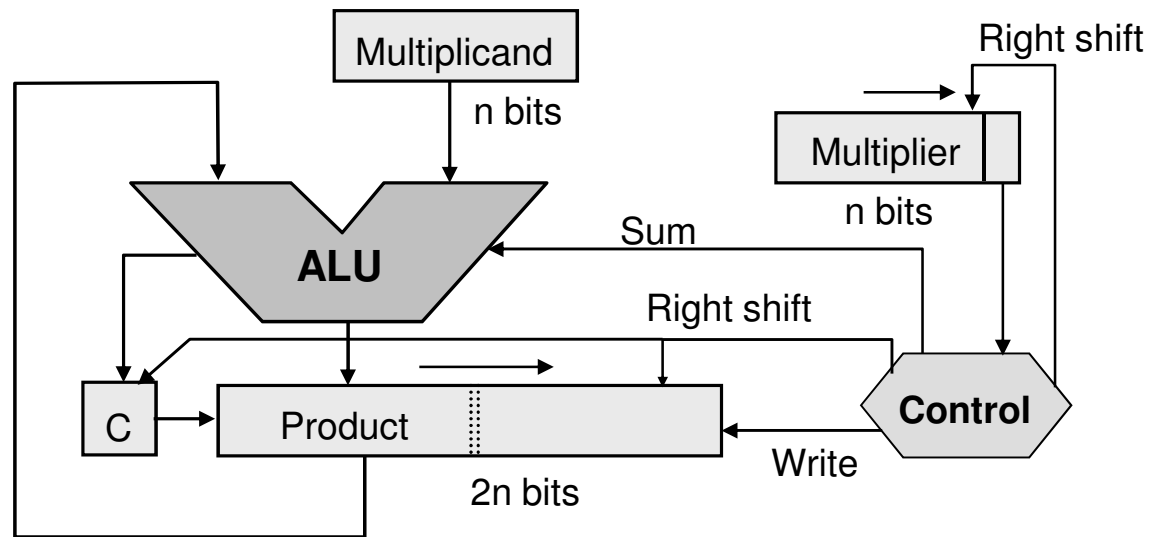



Multiplication

Binary multiplication without sign

Repeat n times

If bit 0 of product register=1 then


Sum the multiplicand to the left half of the product and place the result in the left half of the product.


End if

Shift the product register 1 bit to the right

End repeat


*Final
Version*

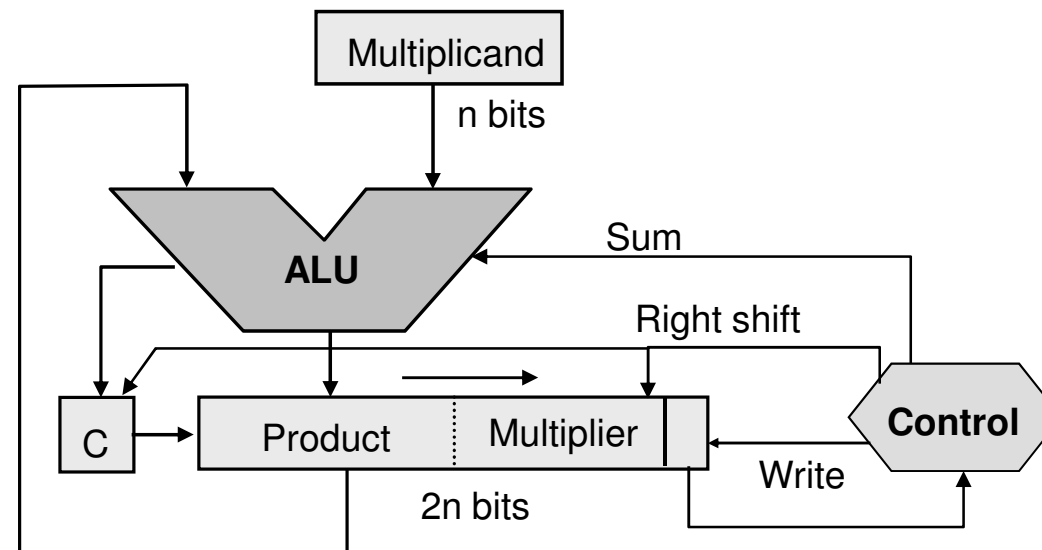


 

Multiplication


Binary multiplication without sign

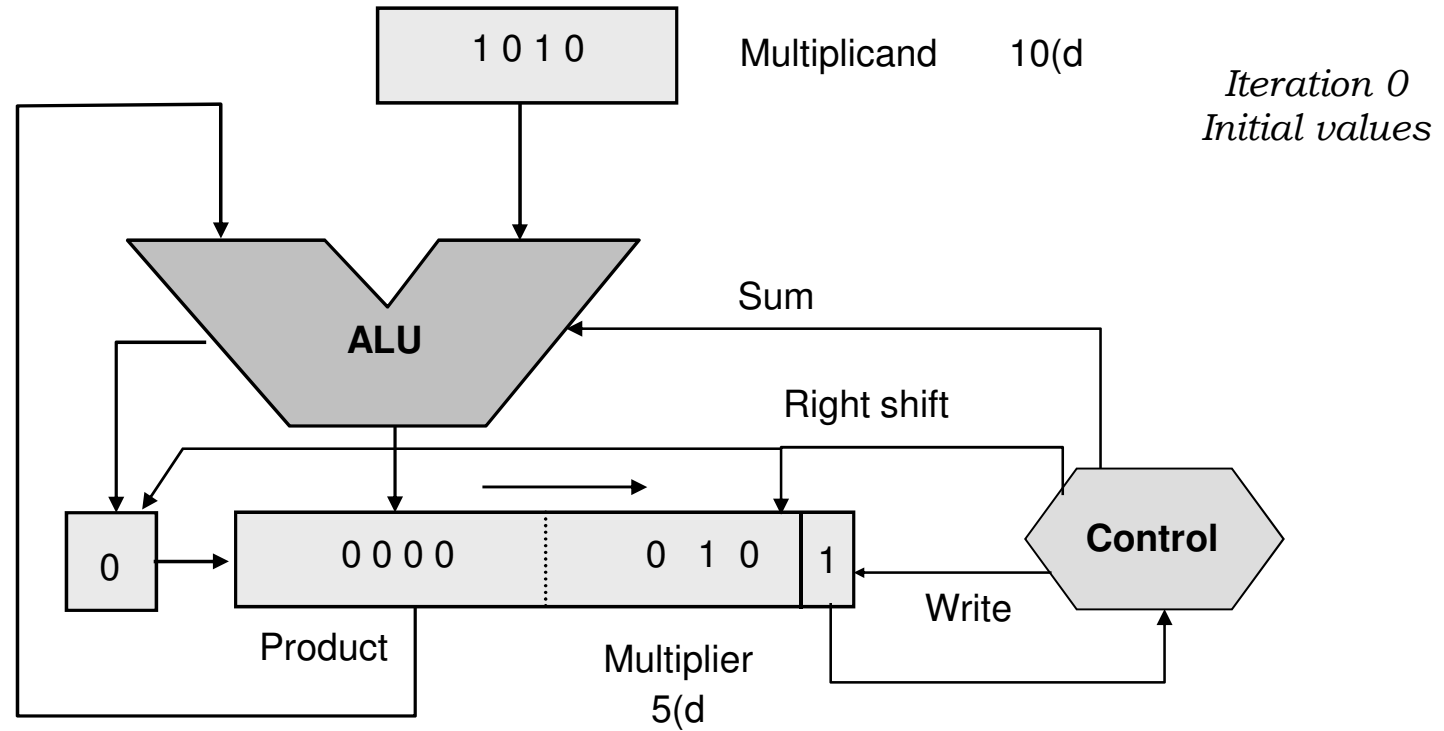


 

Multiplication


Binary multiplication without sign

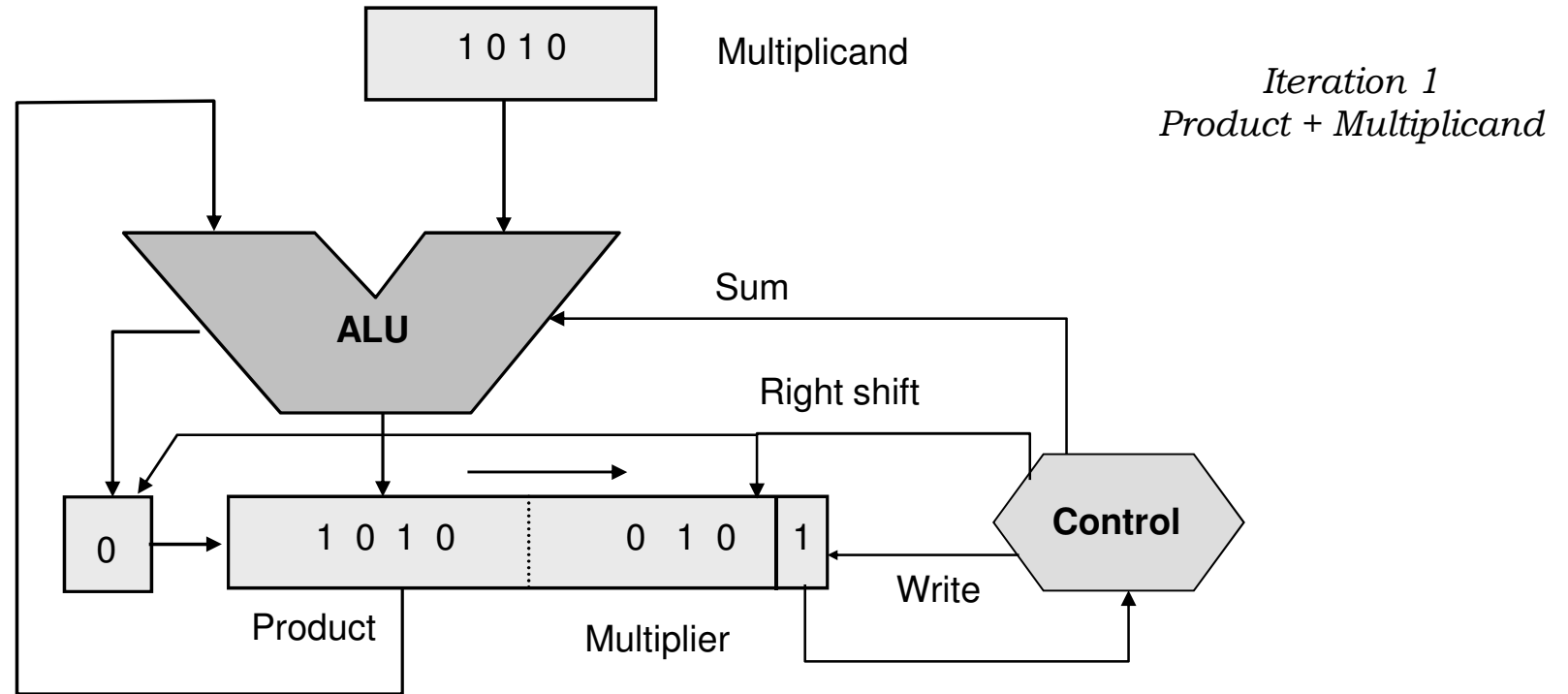


 

Multiplication


Binary multiplication without sign

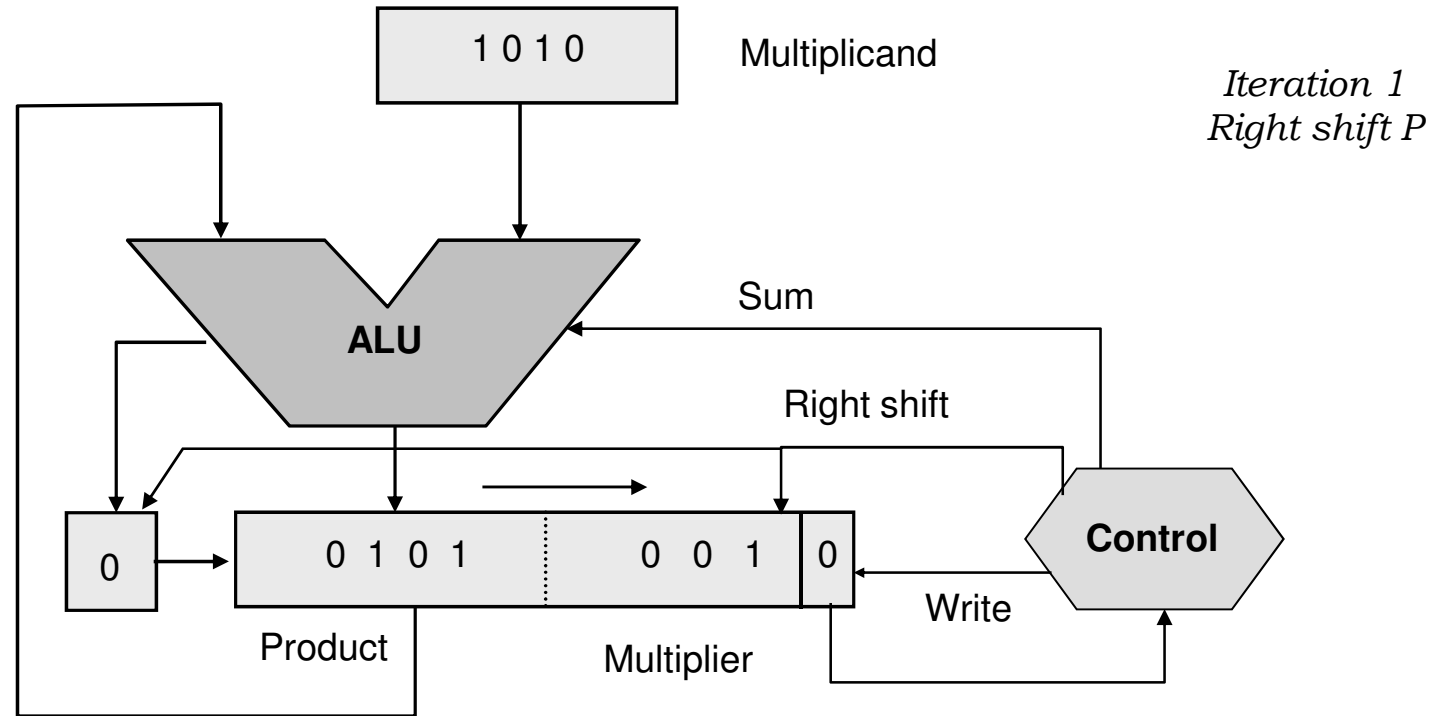


 

Multiplication


Binary multiplication without sign

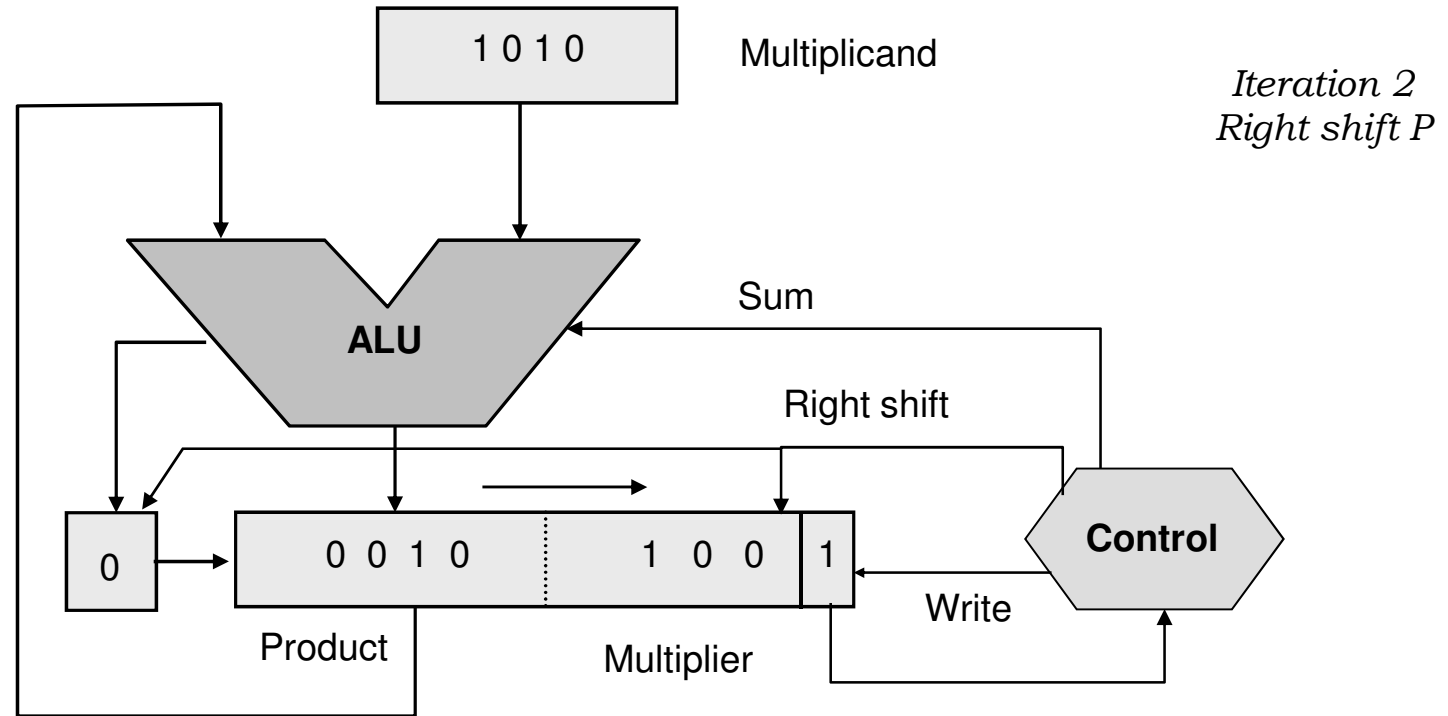


 

Multiplication


Binary multiplication without sign

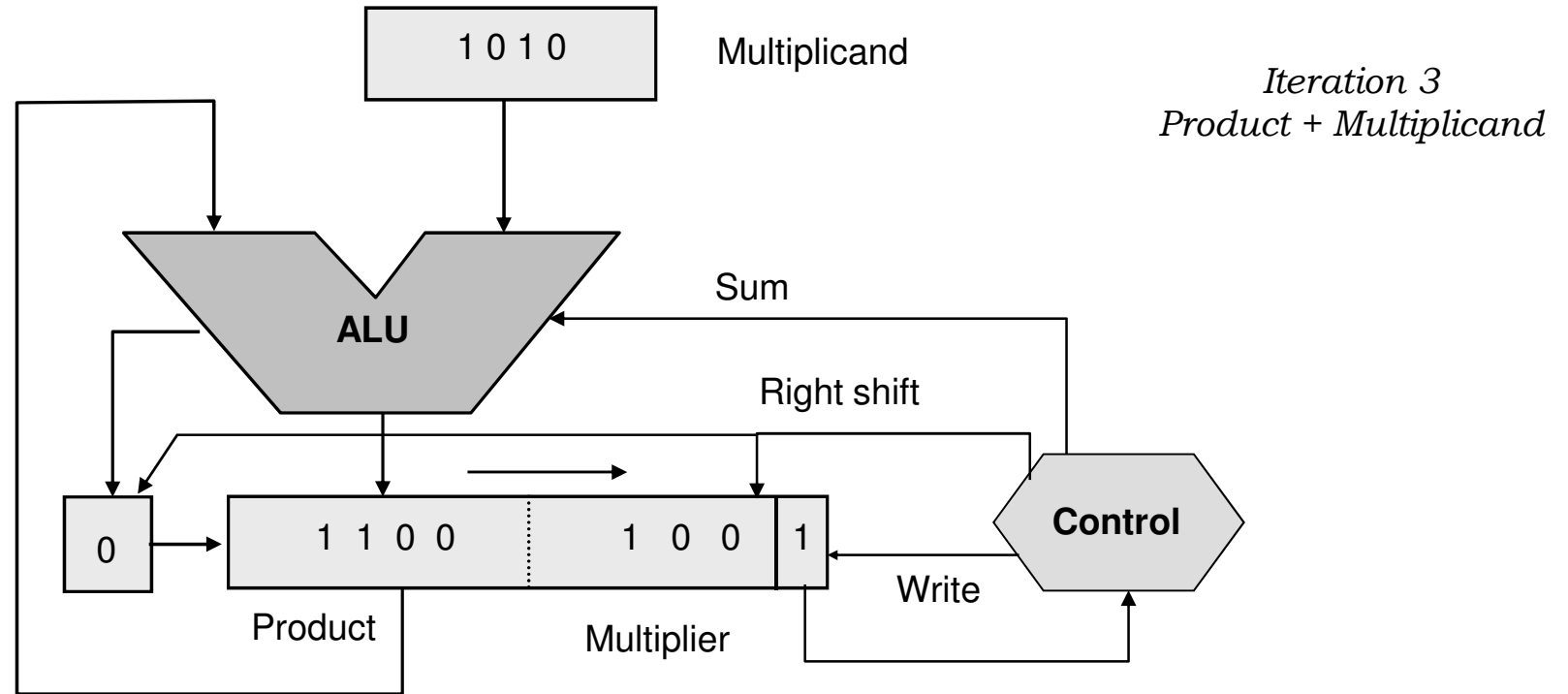


 

Multiplication


Binary multiplication without sign

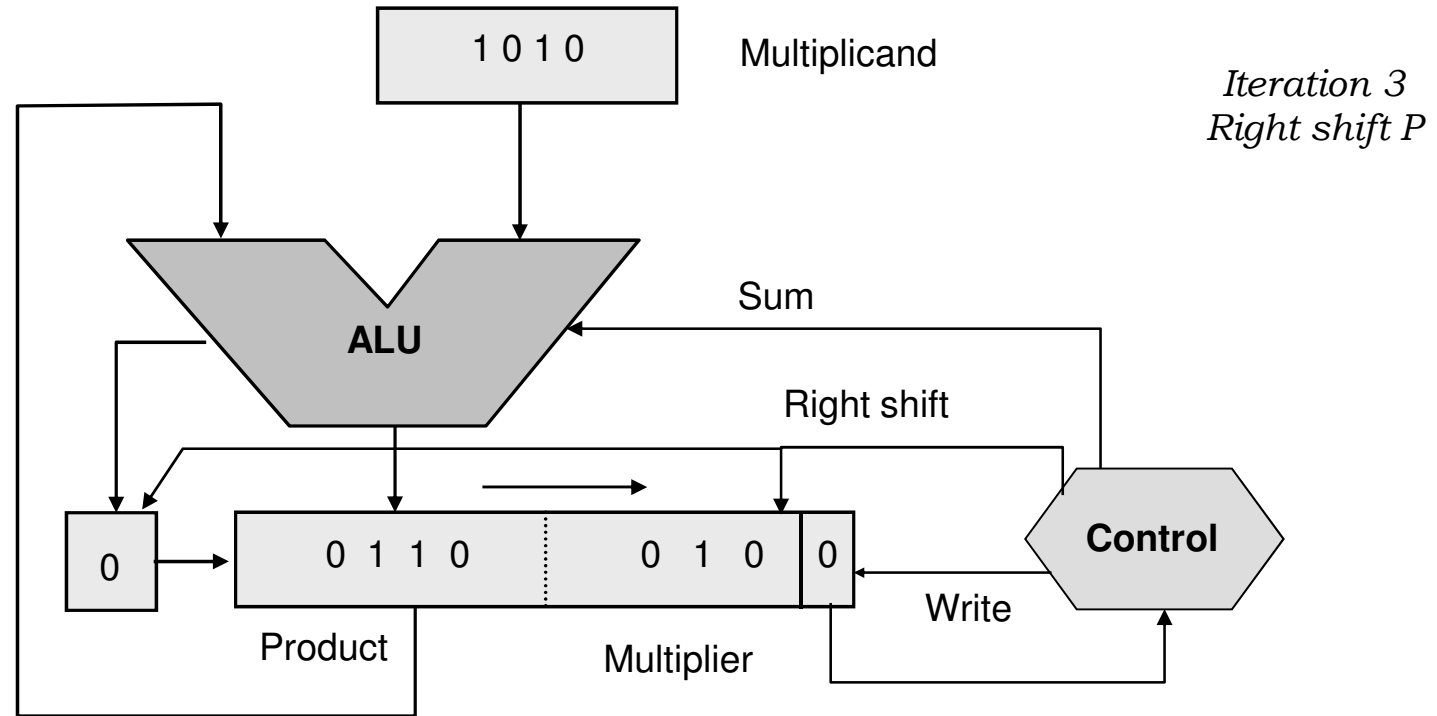

 

Multiplication

Binary multiplication without sign

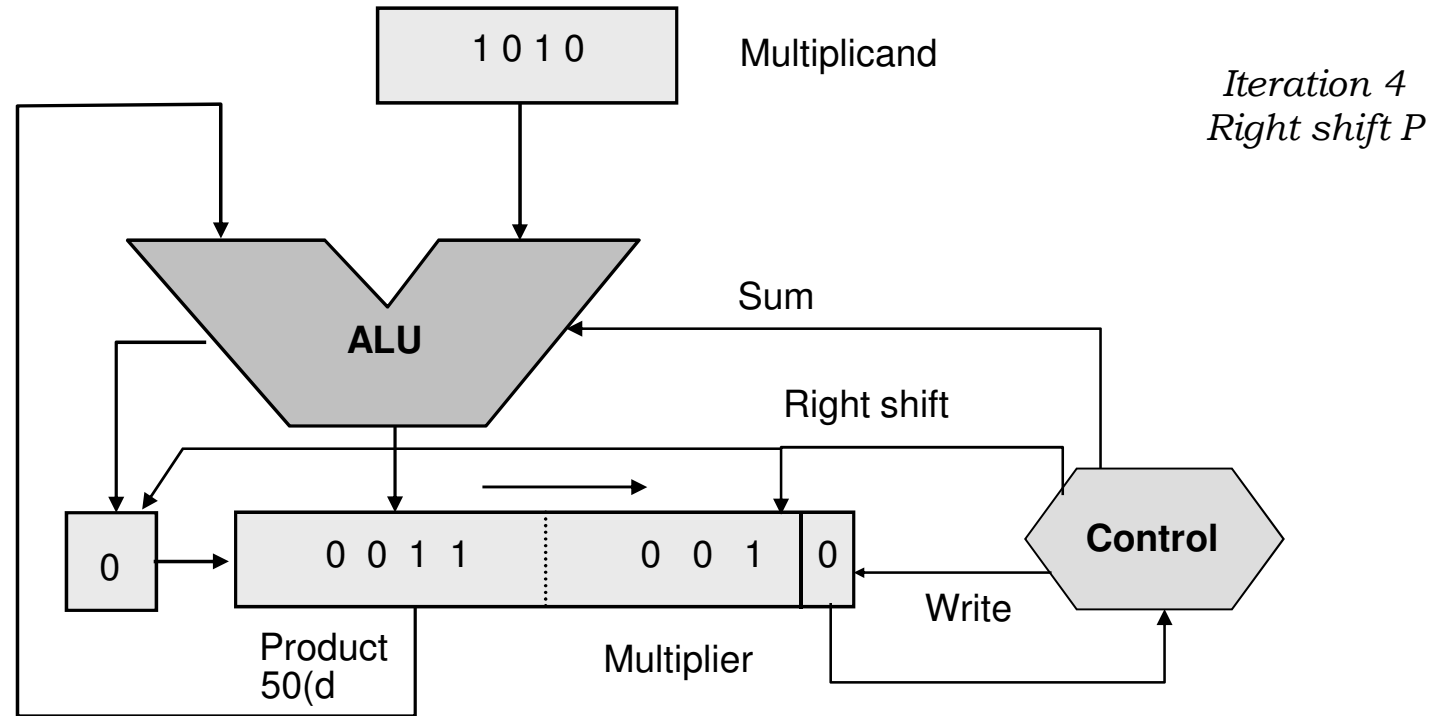




Multiplication

Binary multiplication without sign

Multiplicand = 1010


Multiplier = 0101


Product	Multiplicand	Action	Iteration
0000 0101	1010	Initial values	0
1010 0101	1010	Sum prod. and multiplicand	1
0101 0010	1010	Right shift prod. 1 bit	1
0010 1001	1010	Right shift prod. 1 bit	2
1100 1001	1010	Sum prod. and multiplicand	3
0110 0100	1010	Right shift prod. 1 bit	3
0011 0010	1010	Right shift prod. 1 bit	4

 

Multiplication

Fast multiplication

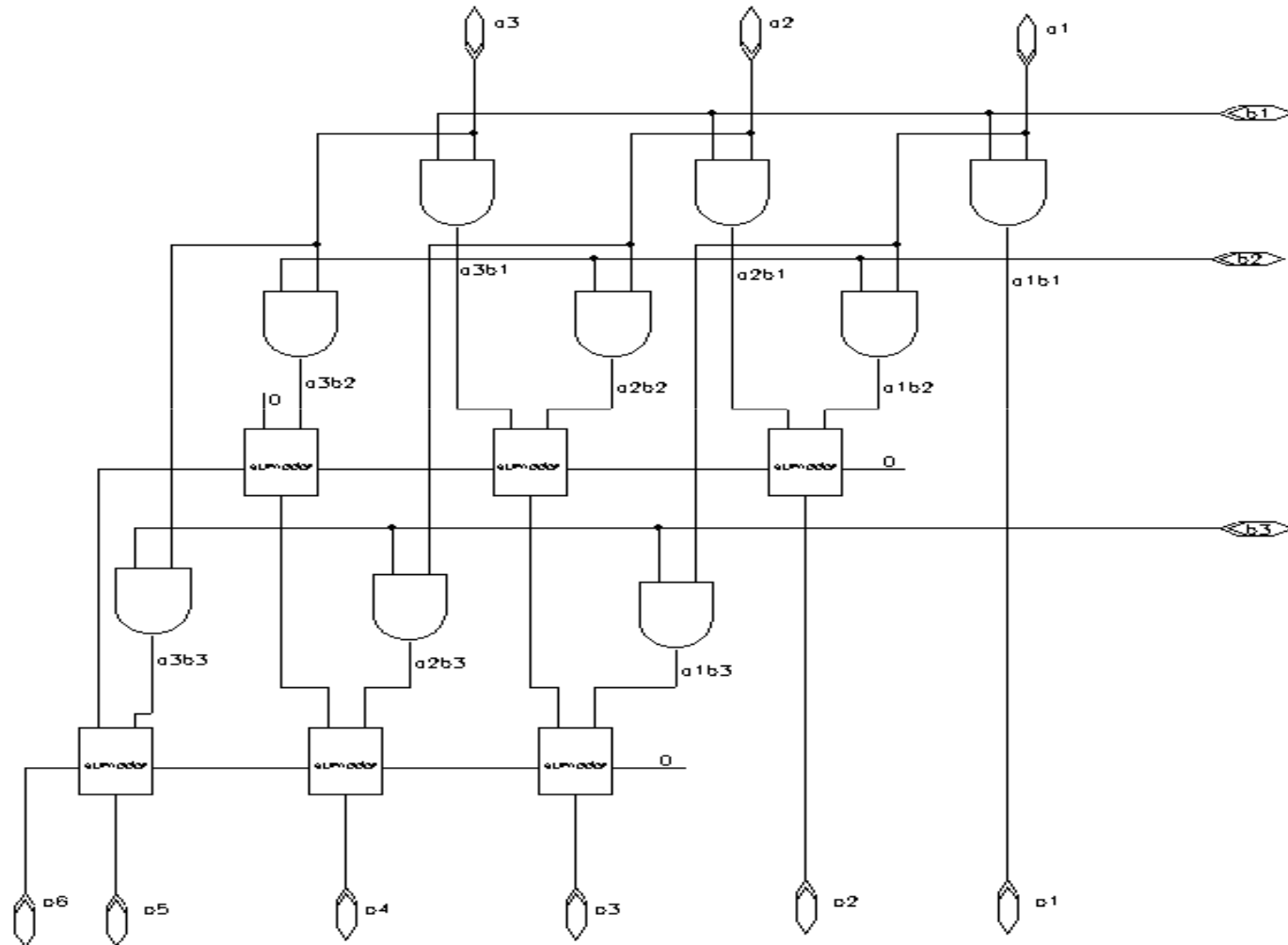

 

Multiplication

Binary multiplication with sign


- ◆ Assume two's complement numbers
- ◆ $A = 1010$ y $B = 0011$
- ◆ Apply sums and shifts algorithm

$$\begin{array}{r} 1010 \\ \times 0011 \\ \hline 1010 \\ 1010 \\ 0000 \\ 0000 \\ \hline 0011110 \end{array}$$

Wrong version

$$\begin{array}{r} 1010 \\ \times 0011 \\ \hline 11111010 \\ 1111010 \\ 000000 \\ 00000 \\ \hline 11101110 \end{array}$$

Right version

 

Multiplication

Booth Algorithm

- ◆ Assume Multiplicand = 2 and Multiplier = 7 (binaries 0010 x 0111)
- ◆ Booth expressed $7 = 8 - 1$ and replaced the multiplier by this decomposition:

$$0111 = 1000 - 0001 = +100-1$$

				0	0	1	0			Multiplicand
			x	+1	0	0	-1			Multiplier according to A. Booth
1	1	1	1	1	1	1	1	0		Multiplicand subtraction
0	0	0	0	0	0	0				2 shifts (2 zeros in the multiplier)
0	0	0	1	0						Multiplicand addition
0	0	0	0	1	1	1	0			




Multiplication

Booth Algorithm

Current Bit	Bit on the left	Replacement
0	0	0 (no transition)
0	1	-1 (transition to negative)
1	0	+1 (transition to positive)
1	1	0 (no transition)

Example: Multiplicand = 11101110 y Multiplier = 01111010
 Multiplier according to Booth = +1000-1+1-10

									1	1	1	0	1	1	1	0
							x	+1	0	0	0	-1	+1	-1	0	
0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	0	0	0	0	0	0	0	1	0	0	1	0	
1	1	1	1	1	1	1	1	1	0	1	1	1	0			
0	0	0	0	0	0	0	0	1	0	0	1	0				
1	1	1	1	0	1	1	1	0	0	0	0					
1	1	1	1	0	1	1	1	0	1	1	0	1	1	0	0	

 

Multiplication

Booth Algorithm

Multiplicand = 1010

Multiplier = 1110

Multiplicand	Product	q ₋₁	Action	Iteration
1010	0000 1110	0	Initial values	0
1010	0000 1110	0	00 → No operation	1
1010	0000 0111	0	Right shift	1
1010	0110 0111	0	10 → Subtraction	2
1010	0011 0011	1	Right shift	2
1010	0011 0011	1	11 → No operation	3
1010	0001 1001	1	Right shift	3
1010	0001 1001	1	11 → No operation	4
1010	0000 1100	1	Right shift	4




Division

Division

- ◆ Division can be expressed as:
$$\text{Dividend} = \text{Quotient} \times \text{Divisor} + \text{Remainder}$$
- ◆ The remainder is smaller than the divisor. Double of space should be reserved for the dividend.
- ◆ Assume positive operands.

$$\begin{array}{r} \text{Dividend} \rightarrow 10010011 \quad | \quad 1011 \quad \leftarrow \text{Divisor} \\ 10010 \quad \quad 01101 \quad \leftarrow \text{Quotient} \\ \hline 1011 \\ 001110 \\ \hline 1011 \\ 001111 \\ \hline 1011 \\ 0100 \quad \leftarrow \text{Remainder} \end{array}$$

 

Division

Algorithm with restoration

Repeat n times

Shift dividend to the left

$\text{Dividend}_h = \text{Dividend}_h - \text{Divisor}$

If $\text{Dividend}_h < 0$ then (does not fit)

$q_0 = 0$


$\text{Dividend}_h = \text{Dividend}_h + \text{Divisor}$ (restore)


else

$q_0 = 1$

end if

end repeat

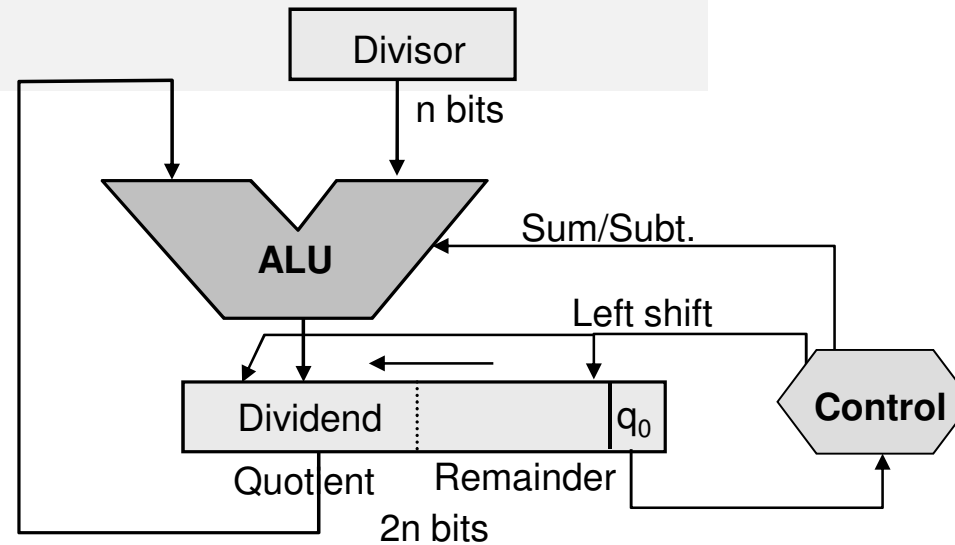

 


Division

Algorithm with restoration

Dividend	Divisor	Action	Iteration
0101 0011	0110	Initial values	0
1010 011_	0110	Shift 1 bit to the left	1
0100 011_	0110	Restar	1
0100 0111	0110	$\text{Dividend}_h > 0 \Rightarrow q_0 = 1$	1
1000 111_	0110	Shift 1 bit to the left	2
0010 111_	0110	$\text{Dividend}_h - \text{Divisor}$ (Subtract)	2
0010 1111	0110	$\text{Dividend}_h > 0 \Rightarrow q_0 = 1$	2
0101 111_	0110	Shift 1 bit to the left	3
1111 111_	0110	$\text{Dividend}_h - \text{Divisor}$ (Subtract)	3
1111 1110	0110	$\text{Dividend}_h \leq 0 \Rightarrow q_0 = 0$	3
0101 1110	0110	$\text{Dividend}_h + \text{Divisor}$ (Restore)	3
1011 110_	0110	Shift 1 bit to the left	4
0101 110_	0110	$\text{Dividend}_h - \text{Divisor}$ (Subtract)	4
0101 1101	0110	$\text{Dividend}_h > 0 \Rightarrow q_0 = 1$	4


↑ ↑
 Rem. Quot.

 


Division

Algorithm without restoration
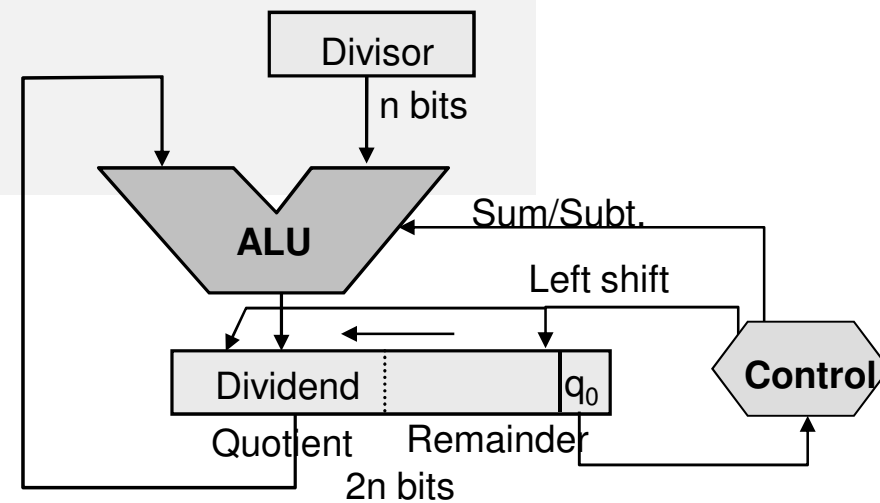
```
Dividendh = Dividendh - Divisor
Repeat n times
  If Dividendh < 0 then
    Shift the Dividend to the left
    Dividendh = Dividendh + Divisor
  Else
    Shift the Dividend to the left
    Dividendh = Dividendh - Divisor
End if
If Dividendh < 0 then
  q0=0
Else
  q0=1
End if
End repeat
```



 

Division

Algorithm without restoration

Dividend	Divisor	Action	Iteration
0000 0111	0010	Initial values	0
1110 0111	0010	$\text{Dividend}_h - \text{Divisor}$	0
1100 111_	0010	$\text{Dividend}_h < 0 \Rightarrow$ Shift left	1
1110 111_	0010	$\text{Dividend}_h + \text{Divisor}$	1
1110 1110	0010	$\text{Dividend}_h < 0 \Rightarrow q_0 = 0$	1
1101 110_	0010	$\text{Dividend}_h < 0 \Rightarrow$ Shift left	2
1111 110_	0010	$\text{Dividend}_h + \text{Divisor}$	2
1111 1100	0010	$\text{Dividend}_h < 0 \Rightarrow q_0 = 0$	2
1111 100_	0010	$\text{Dividend}_h < 0 \Rightarrow$ Shift left	3
0001 100_	0010	$\text{Dividend}_h + \text{Divisor}$	3
0001 1001	0010	$\text{Dividend}_h \geq 0 \Rightarrow q_0 = 1$	3
0011 001_	0010	$\text{Dividend}_h > 0 \Rightarrow$ Shift left	4
0001 001_	0010	$\text{Dividend}_h - \text{Divisor}$	4
0001 0011	0010	$\text{Dividend}_h > 0 \Rightarrow q_0 = 1$	4

↑ ↑

Remain. Quotient



Conclusions

Conclusions

- ◆ Adders
 - ◆ Temporal problems with Carry Propagated Adder, specially if n high.
 - ◆ Carry Look-ahead Adders improve response time of the adders.
- ◆ Multiplication
 - ◆ Problems with the multiplication of signed numbers.
 - ◆ Booth algorithm allows to multiply two's complement numbers and sometimes it reduces the number of operations if there is 1's or 0's chains in the multiplier.
- ◆ Division
 - ◆ Algorithm with restoration for positive numbers. For negative numbers, the sign must be preprocessed. The result's sign will depend on that.